

ICLab Lab04 Exercise

Yu-Fan, Huang

2022 /10 /26



Outline

- **Pipeline Design**

1. Data Flow
2. Critical Issues: Timing and Area
3. Stages

- **Reduce Register and Cycle Count**

1. Reordering pipeline schedule
2. Changing pipeline stages

Pipeline Design: Data Flow

- Data flow:

- $(U * X_1 + W * H_0) \rightarrow \text{sigmoid} \Rightarrow H_1 \rightarrow (V * H_1) \rightarrow \text{relu} \Rightarrow Y_1$
- $(U * X_2 + W * H_1) \rightarrow \text{sigmoid} \Rightarrow H_2 \rightarrow (V * H_2) \rightarrow \text{relu} \Rightarrow Y_2$
- $(U * X_3 + W * H_2) \rightarrow \text{sigmoid} \Rightarrow H_3 \rightarrow (V * H_3) \rightarrow \text{relu} \Rightarrow Y_3$


 


Fig 1. simple RNN

 

$$\begin{aligned} h_1 &= f(U \cdot x_1 + W \cdot h_0) \\ y_1 &= g(V \cdot h_1) \\ h_t &= f(U \cdot x_t + W \cdot h_{t-1}) \\ y_t &= g(V \cdot h_t) \end{aligned}$$

Fig 2. Formula

$$g(x) = \max(0, x)$$

$f(x) = \sigma(x)$

Sigmoid

$$\sigma(x) = \frac{1}{1 + e^{-x}}$$

 


Fig 3.1. The sigmoid activation function

 


Fig 3.2. The ReLU activation function

Pipeline Design: Critical Issues


- Critical Issues: **Timing** and **Area**
 - Matrix Multiplication : Multiply 3 times, Add 2 times (DP3 vs [✓]**MAC**)

(IP)	DP3	MULT + MAC * 2
Cycle time	22ns	5ns~6ns
Cycle Count	1	3


- Sigmoid: *Exp* → *Add* 1 → *Recip* (1 Cycle vs [✓]**3 Cycles**)

(IP)	EXP	ADDER	RECIP
Cycle time	16ns	5ns~6ns	15ns
Cycle Count	1	1	1

Pipeline Design: Stages

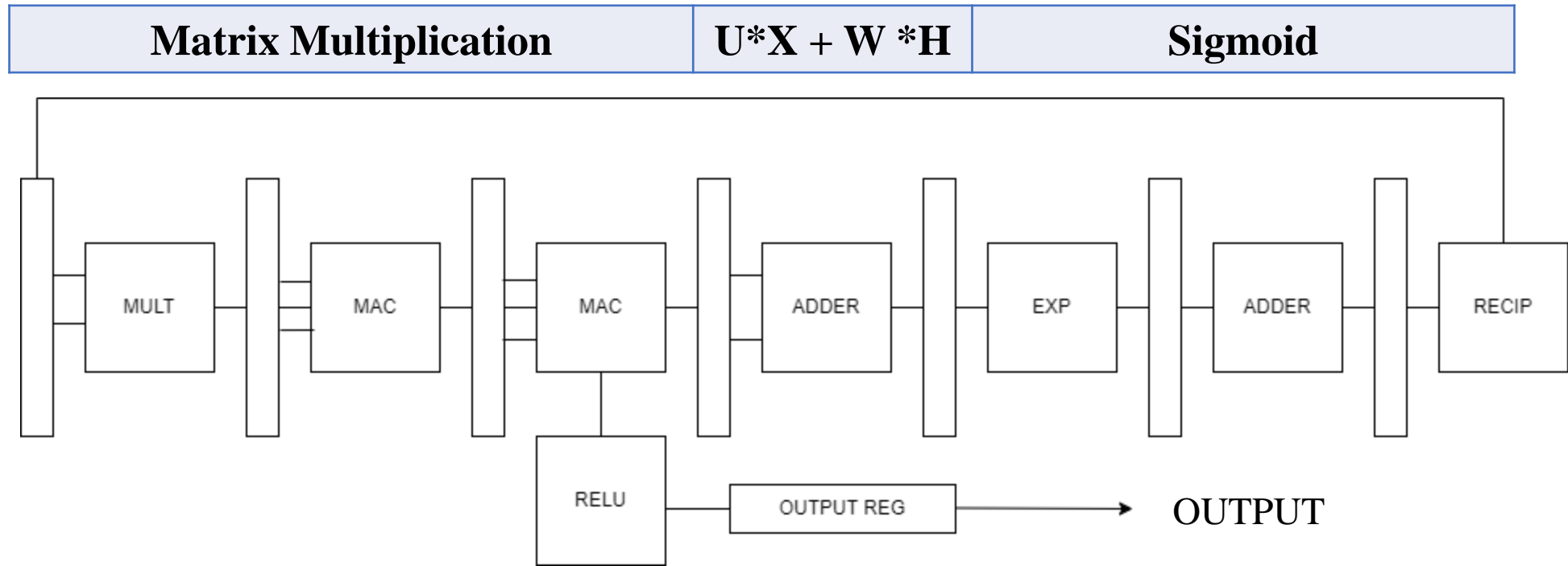


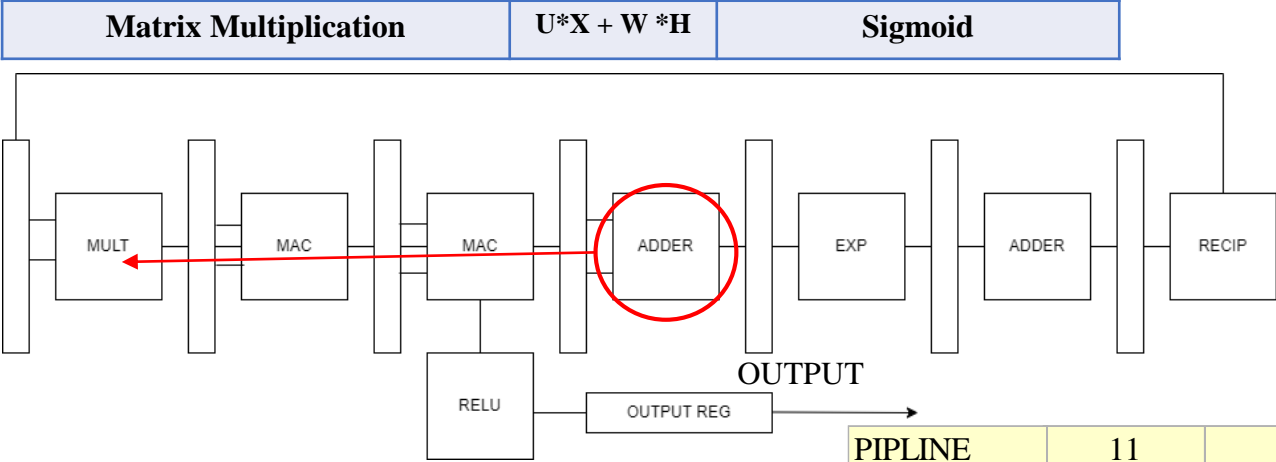Cycle Count Reducing: Changing pipeline stages



PIPELINE	11	12	13	14	15	16	17
Mult 1	$w_{00} * h_{10}$	$w_{10} * h_{10}$	$w_{20} * h_{10}$	$u_{20} * x_{30}$	$v_{00} * h_{10}$	$v_{10} * h_{10}$	$v_{20} * h_{10}$
MAC1	$u_{11} * x_{31}$	$w_{01} * h_{11}$	$w_{11} * h_{11}$	$w_{21} * h_{11}$	$u_{21} * x_{31}$	$v_{01} * h_{11}$	$v_{11} * h_{11}$
MAC2 + Relu	$u_{02} * x_{32}$	$u_{12} * x_{32}$	$w_{02} * h_{12}$	$w_{12} * h_{12}$	$w_{22} * h_{12}$	$u_{22} * x_{32}$	$v_{02} * h_{12}$
	ux_{30}	ux_{31}	wh_{10}	wh_{11}	wh_{12}	ux_{32}	$vh_{10} \rightarrow y_{10}$
Adder1				$wh_{10} + ux_{20}$	$wh_{11} + ux_{21}$	$wh_{12} + ux_{22}$	
				$wh_{10} + ux_{20}$	$wh_{11} + ux_{21}$	$wh_{12} + ux_{22}$	
Exp					$wh_{10} + ux_{20}$	$wh_{11} + ux_{21}$	$wh_{12} + ux_{22}$
					ex_{20}	ex_{21}	ex_{22}
Adder2	$ex_{12} + 1$					$ex_{20} + 1$	$ex_{21} + 1$
	ax_{12}						ax_{20}
Recip		ax_{12}					a_{20}
		$rx_{12} \rightarrow h_{12}$					$rx_{20} \rightarrow h_{20}$

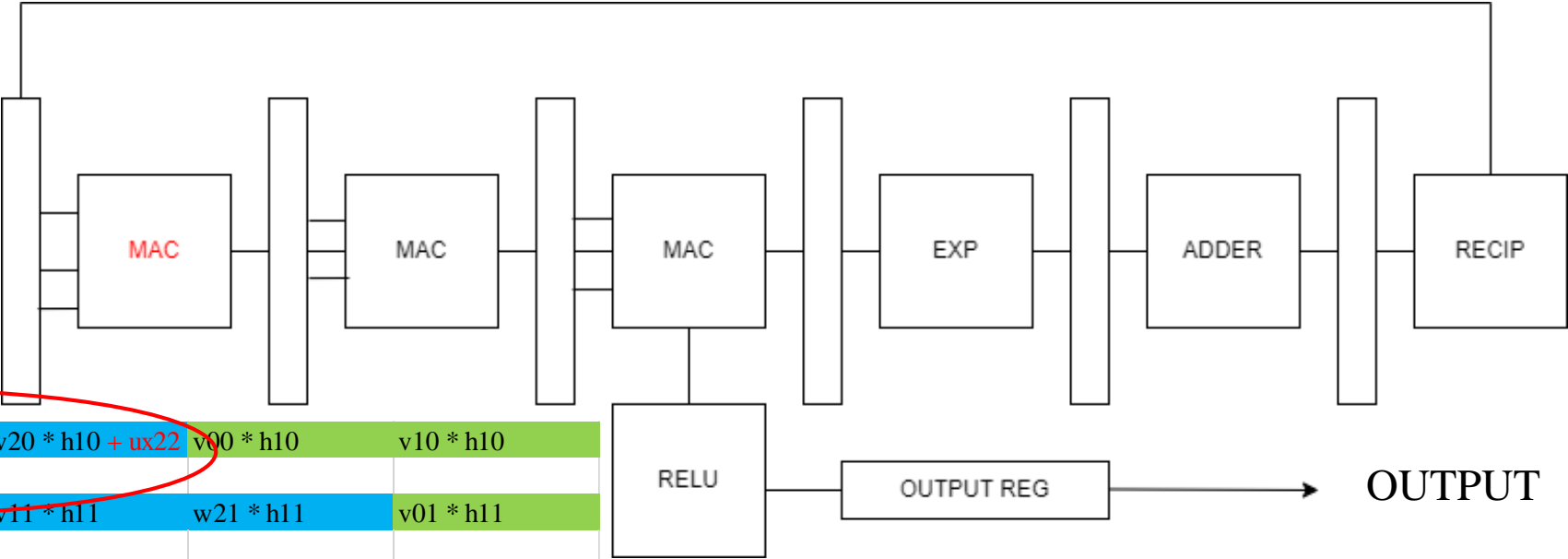Cycle Count Reducing: Changing pipeline stages



Mult adder 1	$w_{00} * h_{10} + ux_{20}$	$w_{10} * h_{10} + ux_{21}$	$w_{20} * h_{10} + ux_{22}$	$v_{00} * h_{10}$	$v_{10} * h_{10}$
Mult adder 2	$u_{21} * x_{31}$	$w_{01} * h_{11}$	$w_{11} * h_{11}$	$w_{21} * h_{11}$	$v_{01} * h_{11}$
Mult adder 3 + Relu	$u_{12} * x_{32}$	$u_{22} * x_{32}$	$w_{02} * h_{12}$	$w_{12} * h_{12}$	$w_{22} * h_{12}$
Exp	ux_{31}	ux_{32}	$wh_{10} + ux_{20}$	$wh_{11} + ux_{21}$	$wh_{12} + ux_{22}$
Add2	$ex_{12} + 1$		ex_{20}	ex_{21}	$ex_{20} + 1$
Recip	ax_{12}	ax_{12}		ax_{20}	
		$rx_{12} \rightarrow h_{12}$			

Reduce Register: Reordering pipeline schedule

- Register Reducing
 - Ex. The result of $(U * X_2)$ and H_2 can store in X_2_reg . X_3_reg can store the result of $(U * X_3)$ and H_3 as well.

4	5	6	7	8	9
u10 * x10	u00 * x20	u10 * x20	u20 * x20	u20 * x10	u00 * x30
u01 * x11	u11 * x11	u01 * x21	u11 * x21	u21 * x21	u21 * x11
	u02 * x12	u12 * x12	u02 * x22	u12 * x22	u22 * x22
	ux10	ux11	ux20	ux21	ux22
		ux10	ux11		
		ex10	ex11		
			ex10 + 1	ex11 + 1	
			ax10	ax11	
				ax10	ax11
				rx10 -> h10	rx11 -> h11

Pipeline

PIPELINE	1	2	3	4	5	6	7	8	9	10	11	12	13	14	15
Mult adder 1			u00 * x10	u10 * x10	u00 * x20	u10 * x20	u20 * x20	u20 * x10	u00 * x30	u10 * x30	u20 * x30	w00 * h10 + ux20	w10 * h10 + ux21	w20 * h10 + ux22	v00 * h10
Mult adder 2				u01 * x11	u11 * x11	u01 * x21	u11 * x21	u21 * x21	u21 * x11	u01 * x31	u11 * x31	u21 * x31	w01 * h11	w11 * h11	w21 * h11
Multa adder 3 + Relu					u02 * x12	u12 * x12	u02 * x22	u12 * x22	u22 * x22	u22 * x12	u02 * x32	u12 * x32	u22 * x32	w02 * h12	w12 * h12
Exp					ux10	ux11	ux20	ux21	ux22	ux12	ux30	ux31	ux32	wh10 + ux20	wh11 + ux21
Add2							ex10 + 1	ex11 + 1					ex12 + 1		wh10 + ux20
Recip							ax10	ax11					ax12		ex20
							rx10 -> h10	rx11 -> h11					rx12 -> h12		

PIPELINE	16	17	18	19	20	21	22	23	24	25	26	27	28	29
Mult adder 1	v10 * h10	v20 * h10	w00 * h20 + ux30	w10 * h20 + ux31	w20 * h20 + ux32	v00 * h20	v10 * h20	v20 * h20	v00 * h30	v10 * h30	v20 * h30			
Mult adder 2	v01 * h11	v11 * h11	v21 * h11	w01 * h21	w11 * h21	w21 * h21	v01 * h21	v11 * h21	v21 * h21	v01 * h31	v11 * h31	v21 * h31		
Multa adder 3 + Relu	w22 * h12	v02 * h12	v12 * h12	v22 * h12	w02 * h22	w12 * h22	w22 * h22	v02 * h22	v12 * h22	v22 * h22	v02 * h32	v12 * h32	v22 * h32	
	wh12 + ux22	vh10 -> y10	vh11 -> y11	vh12- y12	wh20 + ux30	wh21 + ux31	wh22 + ux32	vh20 -> y20	vh21 -> y21	vh22 -> y22	vh30 -> y30	vh31 -> y31	vh32 -> y32	
Exp	wh11 + ux21	wh12 + ux22				wh20 + ux30	wh21 + ux31	wh22 + ux32						
	ex21	ex22				ex30	ex31	ex32						
Add2	ex20 + 1	ex21 + 1	ex22 + 1				ex30 + 1	ex31 + 1	ex32 + 1					
	ax20	ax21	ax22				ax30	ax31	ax32					
Recip		a20	a21	a22				a30	a31	a32				
		rx20 -> h20	rx21 -> h21	rx22 -> h22				rx30 -> h30	rx31 -> h31	rx32 -> h32				
					OUTPUT	y10	y11	y12	y20	y21	y23	y30	y31	y32

Thanks for your attention!